

Copyright © 1985 by W. W. Norton & Company, Inc.

All rights reserved.

Published simultaneously in Canada by Penguin Books Canada Ltd.,  
2801 John Street, Markham, Ontario L3R 1B4.

Printed in the United States of America.

First Edition

Book design by Antonina Krass

Makeup by Roberta Flechner

Production editor Frederick E. Bidgood

Picture research by Amy Boesky and Natalie Goldstein

Library of Congress Cataloging in Publication Data

Ohanian, Hans C.

Physics.

Includes index.

1. Physics. I. Title.

QC21.2.037 1985 530 84-25540

ISBN 0-393-95401-3

W. W. Norton & Company, Inc., 500 Fifth Avenue, New York, N.Y. 10110

W. W. Norton & Company Ltd., 37 Great Russell Street, London WC1B 3NU

1 2 3 4 5 6 7 8 9 0

**Ohmmeter**

registers zero current (the potentiometer is then said to be balanced). Show that if the balance point is at the midpoint of the wire, then  $\mathcal{E}_x = \frac{1}{2} \mathcal{E}_s$ . What if the balance point is at three-quarters of the length of the wire?

10. An **ohmmeter** consists of a standard source of emf (a battery), connected in series with a standard resistance, and an ammeter. When the terminals of the ohmmeter are connected to an unknown resistor (Figure 29.18), the current registered by the ammeter permits the evaluation of the unknown resistance. Explain.

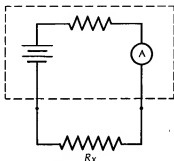


Fig. 29.18

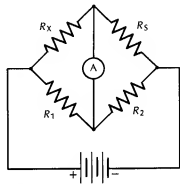


Fig. 29.19

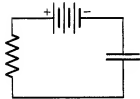
**Wheatstone bridge**

Fig. 29.20

11. The circuit shown in Figure 29.19 is called a **Wheatstone bridge**. It permits a very precise comparison of an unknown resistance with a known, standard resistance. In Figure 29.19 the unknown resistance is  $R_x$ , and the standard resistance is  $R_s$ . The resistances  $R_1$  and  $R_2$  are adjustable. In operation, the resistances  $R_1$  and  $R_2$  are adjusted until the ammeter  $A$  registers zero current. Show that under these conditions the ratios of the resistances are related as follows:  $R_x/R_s = R_1/R_2$ .

12. At  $t = 0$  you connect a battery and a resistor to a capacitor, as shown in Figure 29.20. The capacitor is initially uncharged. Qualitatively, describe the current as a function of time.

13. A homeowner argues that he should not pay his electric bill since he is not keeping any of the electrons that the power company delivers to his home — any electron that enters the wiring of his home sooner or later leaves and returns to the power station. How would you answer?

14. The spiral heating elements commonly used in electric ranges *appear* to be made of metal. Why do they not short circuit when you place an iron pot on them?

15. What are the advantages and what are the disadvantages of high-voltage power lines?

16. In many European countries, electric power is delivered to homes at 220 V, instead of the 110 V customary in the United States. What are the advantages and what are the disadvantages of 220 V?

17. How much does it cost you to operate a 100-watt light bulb for 24 hours? The price of electric energy is 8¢ per kilowatt-hour.

**PROBLEMS****Section 29.1**

1. The smallest batteries weigh 0.05 ounces and store an electric energy of about  $5 \times 10^{-6}$  kW · h. The largest batteries (used aboard submarines) weigh